

BITS-Pilani Dubai Campus
I Sem 2021-22
Digital Design Laboratory / ECE/INSTR/CS F215
Submission Report
Experiment No.- 4 (Adders and Subtractors)


Name: V N Suchir Vangaveeti

ID Number: 2020A7PS0018U

Hardware runs

Run 1: Half adder

Diagram

 


Truth Table

A	B	SUM	CARRY
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Run 2: Half subtractor

Diagram

 

Truth Table

A	B	DIFFERENCE	BORROW
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

Experiment No.- 4 (Adders and Subtractors)

Name: V N Suchir Vangaveeti

ID Number: 2020A7PS0018U

Software runs

Run 3: Full adder and 4-bit adder

Q: Write the Verilog code and testbench of Full adder using data flow modeling.

A: Verilog Code-

```
module fulladder (A,B,C,S,carry);  
    input A,B,C;  
    output S,carry;  
    assign S = A^B^C;  
    assign carry = C & (A^B) | (A&B);  
endmodule
```

```
//testbench  
module fulladder_tb;  
    reg A,B,C;  
    wire S,carry;  
    initial  
    begin  
        $dumpfile("dump.vcd");  
        $dumpvars(1,fulladder_tb);  
        #00 A=0; B=0; C=0;  
        #10 A=0; B=0; C=1;  
        #10 A=0; B=1; C=0;  
        #10 A=0; B=1; C=1;  
        #10 A=1; B=0; C=0;  
        #10 A=1; B=0; C=1;  
        #10 A=1; B=1; C=0;  
        #10 A=1; B=1; C=1;  
        #10 $stop;  
    end  
    fulladder x1(A,B,C,S,carry);  
endmodule
```

Q: Paste the Image of your **Simvision** window where you get the waveforms for the above code.

A:



Experiment No.- 4 (Adders and Subtractors)

Name: V N Suchir Vangaveeti

ID Number: 2020A7PS0018U

Q: Write the Verilog code and testbench for 4- bit parallel adder using structural modeling, use full adder as a building block.

A: Verilog Code-

```
module pfulladder (A,B,S,C,carry);
  input [3:0] A,B;
  input C;
  wire C1, C2, C3;
  output [3:0]S;
  output carry;
  fulladder fa0(C1, S[0], A[0], B[0], C);
  fulladder fa1(C2, S[1], A[1], B[1], C1);
  fulladder fa2(C3, S[2], A[2], B[2], C2);
  fulladder fa3(carry, S[3], A[3], B[3], C3);
endmodule
```

```
module fulladder (A,B,C,S,carry);
  input A,B,C;
  output S,carry;
  assign S=A^B^C;
  assign carry=C&(A^B)|(A&B);
endmodule
```

```
//testbench
module pfulladder_tb;
  reg[3:0]A,B;
  wire carry;
  wire [3:0]S;
  initial
  begin
    $dumpfile("dump.vcd");
    $dumpvars(1,pfulladder_tb);
    #00 A=4'b0001; B=4'b0010;
    #10 A=4'b1101; B=4'b1010;
    #10 A=4'b0110; B=4'b1010;
    #10 A=4'b0101; B=4'b1110;
    #10 A=4'b1101; B=4'b1010;
    #10 A=4'b0110; B=4'b0010;
    #10 $stop;
  end
  pfulladder FA1(A,B,S,C,carry);
endmodule
```


Experiment No.- 4 (Adders and Subtractors)

Name: V N Suchir Vangaveeti

ID Number: 2020A7PS0018U


Q: Paste the Image of your **Simvision** window where you get the waveforms for the above code.

A:

 

Run 4: BCD adder

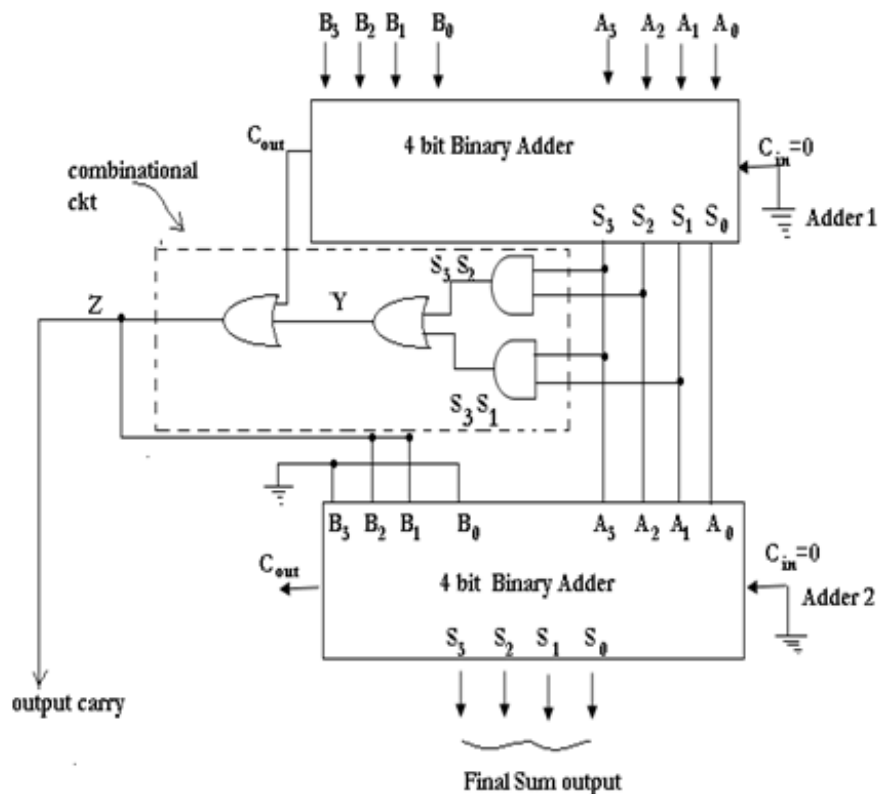Q: Write the verilog code and testbench for BCD adder using structural modeling, use 4-bit parallel adder and other gates as building blocks. (Hint refer the image below)



A: Verilog Code-

```
module bcd_adder(carry,secondB, sum, a, b);
input[3:0] a,b;
output[3:0] sum;
output carry;
reg ip=0;
wire[3:0] s;
wire[1:0] op;
```

Experiment No.- 4 (Adders and Subtractors)

Name: V N Suchir Vangaveeti

ID Number: 2020A7PS0018U

```
output reg[3:0] secondB;
paralleladder g1 (op[0], s, a, b, ip);
assign carry = s[1]&s[3] | s[2]&s[3] | op;
assign secondB[0] = 0;
assign secondB[1] = carry;
assign secondB[2] = carry;
assign secondB[3] = 0;
paralleladder g2 (op[1], sum, s, secondB, ip);
endmodule
```

```
module paralleladder(op, sum, a, b, iip);
input[3:0] a,b;
input iip;
output[3:0] sum;
output op;
wire[2:0] ip;
fulladder G1 (ip[0], sum[0], a[0], b[0], iip);
fulladder G2 (ip[1], sum[1], a[1], b[1], ip[0]);
fulladder G3 (ip[2], sum[2], a[2], b[2], ip[1]);
fulladder G4 (op, sum[3], a[3], b[3], ip[2]);
endmodule
```

```
module fulladder (op, sum, a, b, ip );
input a,b,ip;
output op, sum;
assign sum = a^b^ip;
assign cout = ip&(a^b) | a&b;
endmodule
```

```
//testbench
module testbench();
reg[3:0] a,b;
wire[3:0] sum,secondB;
wire carry;
initial begin
$dumpfile ("dump.vcd");
$dumppvars (1, testbench);
#000 a = 4'b0000; b = 4'b0000;
#100 a = 4'b1001; b = 4'b0011;
#100 a = 4'b1000; b = 4'b1000;
#100 a = 4'b1000; b = 4'b0111;
#100 a = 4'b0101; b = 4'b0111;
#100 a = 4'b0000; b = 4'b0000;
#100;
```

Experiment No.- 4 (Adders and Subtractors)

Name: V N Suchir Vangaveeti

ID Number: 2020A7PS0018U

```
$stop;  
end  
bcd_adder g1 (carry,secondB, sum, a, b);  
endmodule
```

Q: Paste the Image of your **Simvision** window where you get the waveforms for the above code.

A:



Assignment All assignments are to be submitted strictly before start of next lab session through online only. Late assignments will not be entertained and will be awarded '0' marks.

Copy-paste or type the unique URL of your assignment solution from website www.edaplayground.com for assignment questions. Please note that do not copy someone else's link as any kind of unfair means will result in academic misconduct and will be treated accordingly. All links for each user and each code are unique.

Q1: Verilog code and testbench for converting 8-bit binary number to gray code using data flow modeling.

Ans: Link1: <https://edaplayground.com/x/EcGD>

Q2: Verilog code and testbench for full subtractor using data flow modeling.

Ans: Link2: <https://edaplayground.com/x/Wpcn>

Q3: Verilog code and testbench for full subtractor using behavioral modeling.

Ans: Link3: <https://edaplayground.com/x/hcCW>