

BITS-Pilani Dubai Campus
I Sem 2021-22
Digital Design Laboratory / ECE/INSTR/CS F215
Submission Report
Experiment No.- 6 (Multiplexer and Demultiplexer)


Name: V N Suchir Vangaveeti

ID Number: 2020A7PS0018U

Hardware runs

Run 1: Multiplexer

Diagram

 

Truth Table

S	C	B	A	Y	Y'
1	x	x	x	x	x
0	0	0	0	1	0
0	0	0	1	0	1
0	0	1	0	0	1
0	0	1	1	0	1
0	1	0	0	1	0
0	1	0	1	0	1
0	1	1	0	1	0
0	1	1	1	0	1


Experiment No.- 6 (Multiplexer and Demultiplexer)

Name: V N Suchir Vangaveeti

ID Number: 2020A7PS0018U

Run 2: Demultiplexer

Diagram

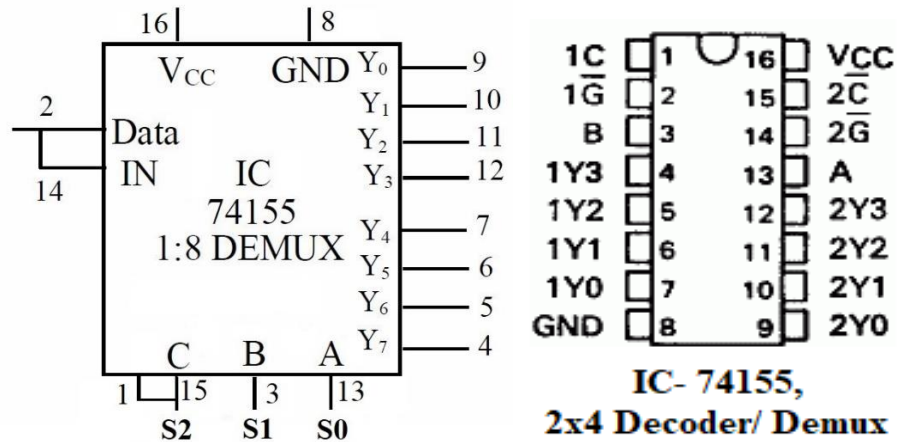

Truth Table

Data	C	B	A	Y0	Y1	Y2	Y3	Y4	Y5	Y6	Y7
1	0	0	0	1	1	1	1	1	1	1	1
0	0	0	1	1	0	1	1	1	1	1	1
0	0	1	0	1	1	0	1	1	1	1	1
0	0	1	1	1	1	1	0	1	1	1	1
1	1	0	0	1	1	1	1	1	1	1	1
0	1	0	1	1	1	1	1	1	0	1	1
1	1	1	0	1	1	1	1	1	1	1	1
0	1	1	1	1	1	1	1	1	1	1	0

Experiment No.- 6 (Multiplexer and Demultiplexer)

Name: V N Suchir Vangaveeti

ID Number: 2020A7PS0018U

Software runs

Run 3: Multiplexer


1. Write the Verilog code and testbench for 2:1 Multiplexer using data flow modeling

A: Verilog Code and testbench-

```
module run3 (y,i,s0 );
  input[1:0] i;
  input s0;
  output y;
  wire p,q;
  assign p = i[0] & ~s0;
  assign q = i[1] & s0;
  assign y = p | q;
endmodule
```

```
//testbench
module testbench();
  reg[1:0] i;
  reg s0;
  wire y;
  initial begin
    #000 i=2'b00; s0=1;
    #100 i=2'b00; s0=0;
    #100 i=2'b01; s0=0;
    #100 i=2'b10; s0=0;
    #100 i=2'b11; s0=0;
    #100 i=2'b00; s0=1;
    #100 i=2'b01; s0=1;
    #100 i=2'b10; s0=1;
    #100 i=2'b11; s0=1;
    # 100 $stop;
  end run3 g1 (y,i,s0);
endmodule
```

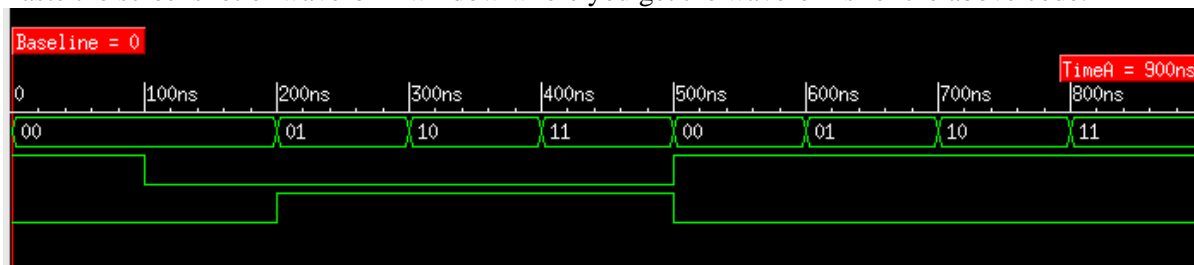Q: Paste the screenshot of waveform window where you get the waveforms for the above code.



A:

Experiment No.- 6 (Multiplexer and Demultiplexer)

Name: V N Suchir Vangaveeti

ID Number: 2020A7PS0018U


2. Write the Verilog code and testbench for 4:1 Multiplexer using behavioral modeling.

A: Verilog Code and testbench -

```
module run32 (  
input i0,i1,i2,i3, s0,s1,  
output reg y);  
always @ (*) begin  
case ({s0,s1})  
2'b00; y = i0;  
2'b01; y = i1;  
2'b10; y = i2;  
2'b11; y = i3;  
endcase  
end  
endmodule  
  
//testbench  
module testbench();  
reg i0,i1,i2,i3,s0,s1;  
wire y;  
initial begin  
#000 i0=0; i1=0; i2=0; i3=0; s0=0; s1=0;  
#100 i0=0; i1=1; i2=0; i3=1; s0=0; s1=0;  
#100 i0=0; i1=1; i2=0; i3=1; s0=0; s1=1;  
#100 i0=0; i1=1; i2=0; i3=1; s0=1; s1=0;  
#100 i0=0; i1=1; i2=0; i3=1; s0=1; s1=1;  
#100 $stop;  
end  
run32 g1 ( i0,i1,i2,i3, s0,s1, y);  
endmodule
```

Q: Paste the screenshot of waveform window where you get the waveforms for the above code.

A:

 

Experiment No.- 6 (Multiplexer and Demultiplexer)

Name: V N Suchir Vangaveeti

ID Number: 2020A7PS0018U

3. Write the Verilog code and testbench for 4:1 Multiplexer using structural modeling.

A: Verilog Code and testbench -


```
module run33 (d,q,s);
output q;
input[3:0] d;
input[1:0] s;
wire one,two;
t2x1mux g1 (one,d[0], d[1], s[0]);
t2x1mux g2 (two,d[2], d[3], s[0]);
t2x1mux g3 (q,one, two, s[1]);
endmodule
```

```
module t2x1mux (y,i0,i1,s0 );
input i0,i1;
input s0;
output y;
wire p,q;
assign p = i0 & ~s0;
assign q = i1 & s0;
assign y = p|q;
endmodule
```

```
//testbench
module testbench();
wire q;
reg[3:0] d;
reg[1:0] s;
initial begin
#000 d=4'b0000; s=2'b00;
#100 d=4'b0101; s=2'b01;
#100 d=4'b0101; s=2'b10;
#100 d=4'b0101; s=2'b11;
#100 $stop;
end
run33 g1 (d,q,s);
endmodule
```

Q: Paste the screenshot of waveform window where you get the waveforms for the above code.

A:

 

Experiment No.- 6 (Multiplexer and Demultiplexer)

Name: V N Suchir Vangaveeti

ID Number: 2020A7PS0018U

Run 4: Demultiplexer

1. Write the Verilog code and testbench for 1:4 demultiplexer using behavioral modeling.


A: Verilog Code and testbench -

```
module run41 (input din, s0,s1, output o0, o1, o2, o3);  
assign o0 = din & (~s1 & ~s0);  
assign o1 = din & (~s1 & s0);  
assign o2 = din & (s1 & ~s0);  
assign o3 = din & (s1 & s0);  
endmodule
```

```
//testbench  
module testbench();  
reg din;  
reg s[1:0];  
wire[3:0] o;  
initial begin  
#000 din = 0; s[1] = 0; s[0] = 0;  
#100 din = 1; s[1] = 0; s[0] = 0;  
#100 din = 1; s[1] = 0; s[0] = 1;  
#100 din = 1; s[1] = 1; s[0] = 0;  
#100 din = 1; s[1] = 1; s[0] = 1;  
#100 $stop;  
end  
run41 g1 (din,s[0],s[1],o[0],o[1],o[2],o[3]);  
endmodule
```

Q: Paste the screenshot of waveform window where you get the waveforms for the above code

A:

 

Experiment No.- 6 (Multiplexer and Demultiplexer)

Name: V N Suchir Vangaveeti

ID Number: 2020A7PS0018U

Assignment All assignments are to be submitted strictly before start of next lab session through online only. Late assignments will not be entertained and will be awarded '0' marks.

1. Write the Verilog code and testbench for 4:1 Multiplexer using data flow modeling.

Ans: Link1: <https://edaplayground.com/x/BfVP>

2. Verilog code and testbench for implementing 2-input XOR gate using 2x1 multiplexer in structural modeling.

Ans: Link2: <https://edaplayground.com/x/7WjK>

Self-Practice and self-evaluation

1. Verilog code and testbench for implementing 2-input NAND gate using 2x1 multiplexer in structural modeling.
2. Verilog code and testbench for a 4-input 4-output 1-channel communication system using 4x1 multiplexer and 1x4 demultiplexer, control the select lines of multiplexer and demultiplex to switch the channel data between 4-input lines.
3. Verilog code and testbench for 8x1 multiplexer using 4x1 multiplexer and 2x1 multiplexer in structural modeling.